

Name and Student ID: ARYAN RAO, 264954748

Lab Section: 11

Date: 12/01/2022

Submission Instructions:

Prelab:

1. No prelab


Lab:

1. Complete the scavenger hunt according to the instructions
2. Take screenshots of each component and include them in the document below (note: to receive points your NetID has to be visible in the screenshot, say in a command window that is in the background).
3. Complete this document and upload it to Canvas

LAB: CPU Scavenger Hunt

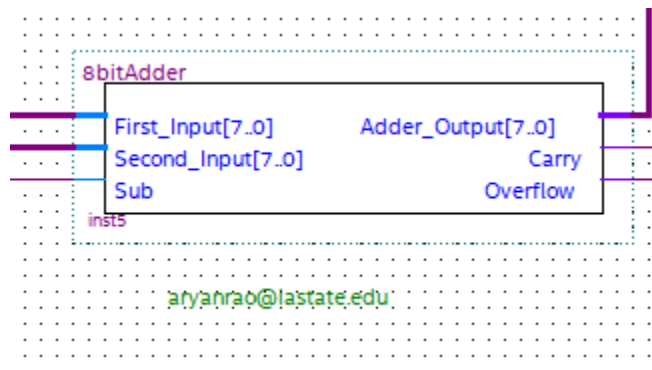
Q1. Find the **adder** inside the ALU and answer the following:

- What is the name of this component?
It is an 8-BIT Adder
- Is it a ripple-carry or carry lookahead adder?
It is a ripple-carry adder.
- Can it also do subtraction?
It can do subtraction.
- What is the size of its two operands in bits?
Each operand is 8 bits.



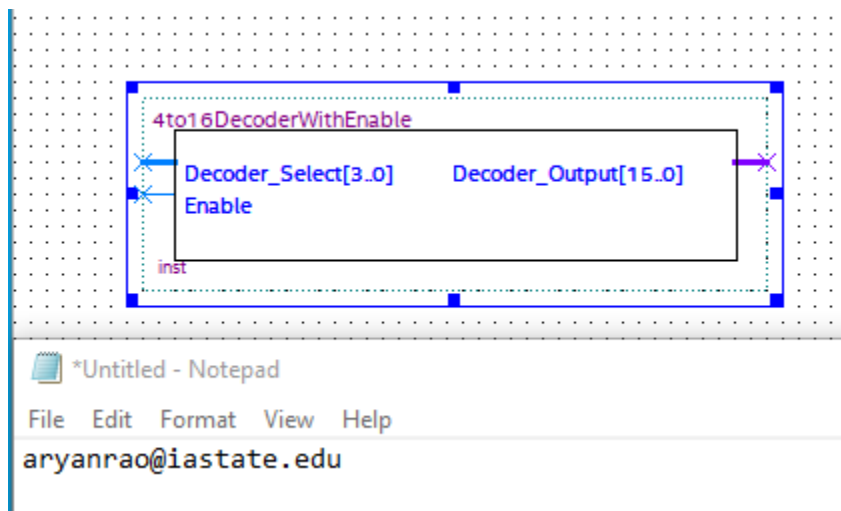
Q2. Find a 4-to-16 **decoder** and answer the following:

- What is the name of this component?
4-16 Decoder with enable
- Does it have an enable input?
Yes, it has an enable input
- What are the names of its outputs 4 and 6?
Since counting starts at 0, output 4 is Decoder_ouput3 and output 6 is Decoder_Output5
- Can you guess what is its function in this CPU?
The decoder is used to select which register is going to get changed. It accepts a number from 0-15 and the decoder then activates that line which enables that register so that it can be written to.



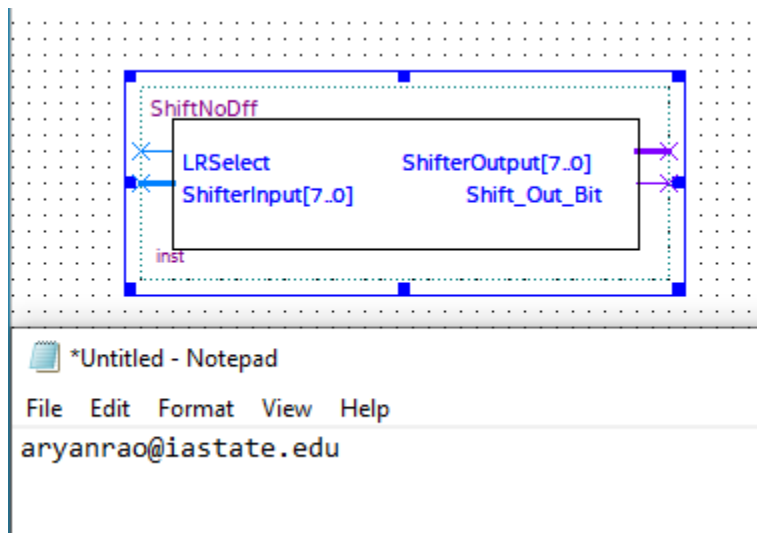
Q3. Find a **shifter circuit** and answer the following:

- What is the name of this component?
8- BIT Shifter inside ALU(ShiftNoDiff)
- What is the size of the input in bits?
Shifter has capacity of 8 BITS
- What happens to the most significant bit on shift left?
It gets shifted out
- What happens to the least significant bit on shift right?
It also gets shifted out



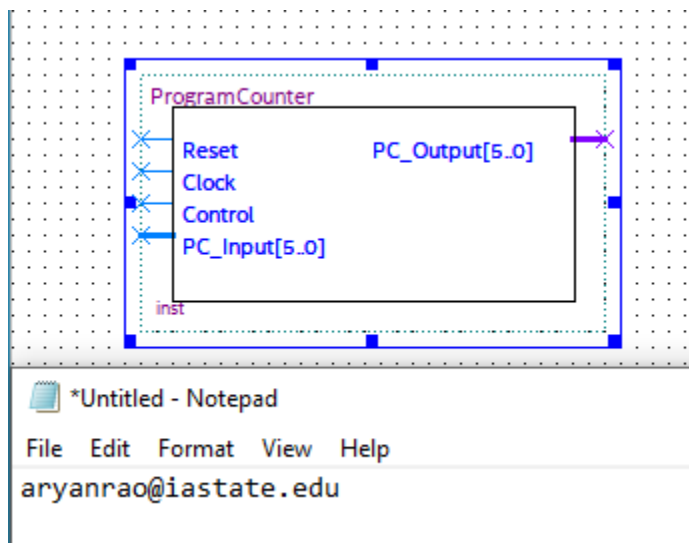
Q4. Find the **program counter** and answer the following:

- What is the name of this component?
It is called a Program Counter(inst)
- What is the size of the output bus in bits?
Output is 6 bits long.
- How many control lines does it have?
It has 1 control line, 1 reset and 1 clock for a total of 3 control lines.
- What type of high-level circuit does it implement?
It implements a register file since it has DFF and MUXes which control if it can be written to or not



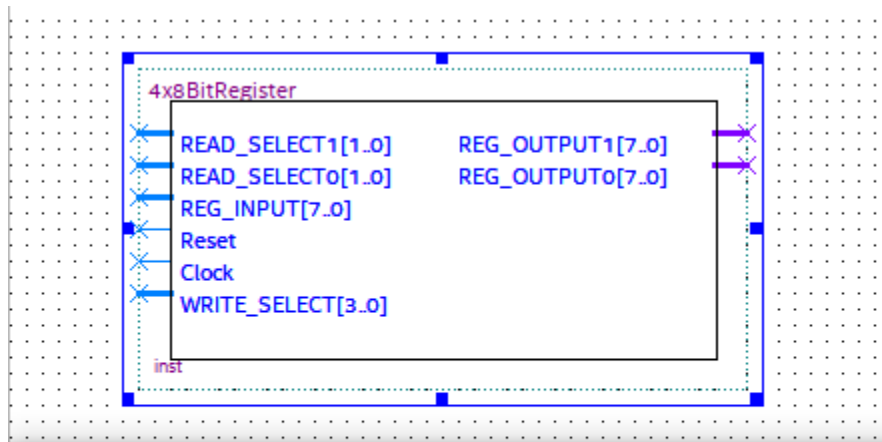Q5. Find a **register file** with exactly 4 registers and answer the following:

- What is the name of this component?
The IMEM component has 4 registers, 2 BIOS and 2 Instructions.
- What is the size of each register in bits?
The registers are 16 bits wide and there are 16 16-bit registers. There are 4 of them. The total memory is $16 \times 16 \times 4$ for a total of 1024 bits.
- What type of Flip-Flops are used to construct each register?
Positive Edge triggered D- Flip Flops are used
- The contents of how many registers can be read at the same time?
2 Registers can be read at the same time.




*Untitled - Notepad

File Edit Format View Help

aryanrao@iastate.edu

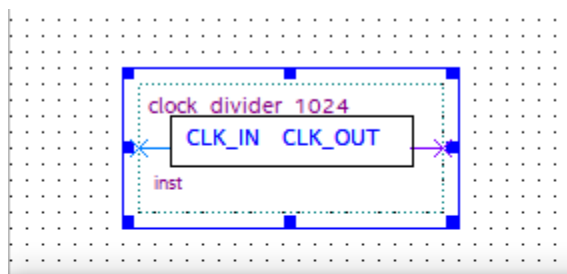Q6. Find the two **clock dividers** for the **VideoGame_Clock** and answer the following:

- How are they implemented?
They are implemented by using multiple synchronous down counters which helps to slow the clock down.
- They slow down the clock by a factor of X and Y. What are X and Y?
The first one divides it by $2^{10} = 1024$ and the other divides it by $2^9 = 512$




*Untitled - Notepad

File Edit Format View Help

aryanrao@iastate.edu

•

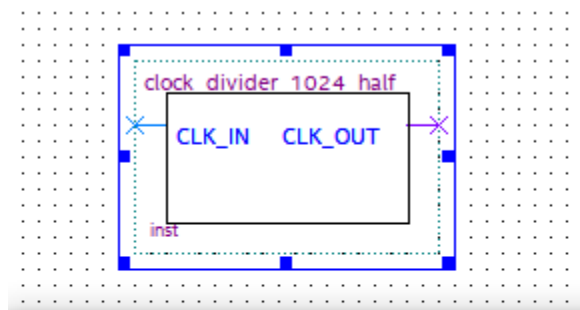

*Untitled - Notepad


File Edit Format View Help

aryanrao@iastate.edu

•

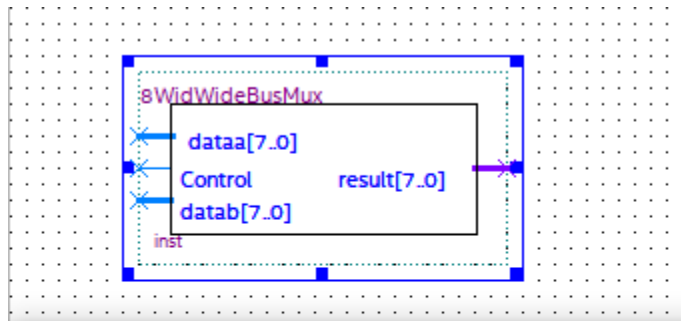Q7. Find the **multiplexer** that sits after the ALU and takes the output of the ALU as one of its inputs. Then, answer the following:

- What is the name of this component?
It is an 8 bit bus 2-1 MUX(8WidWideBusMux)
- Where does the other input come from?
The other input to the mux are the lower 8 bits of the output of IMEM.
- What is the size of each input in bits?
Size of each input is 8 bits
- How many select lines does it have in bits?
It has 1 select line



*Untitled - Notepad


File Edit Format View Help

aryanrao@iastate.edu

•

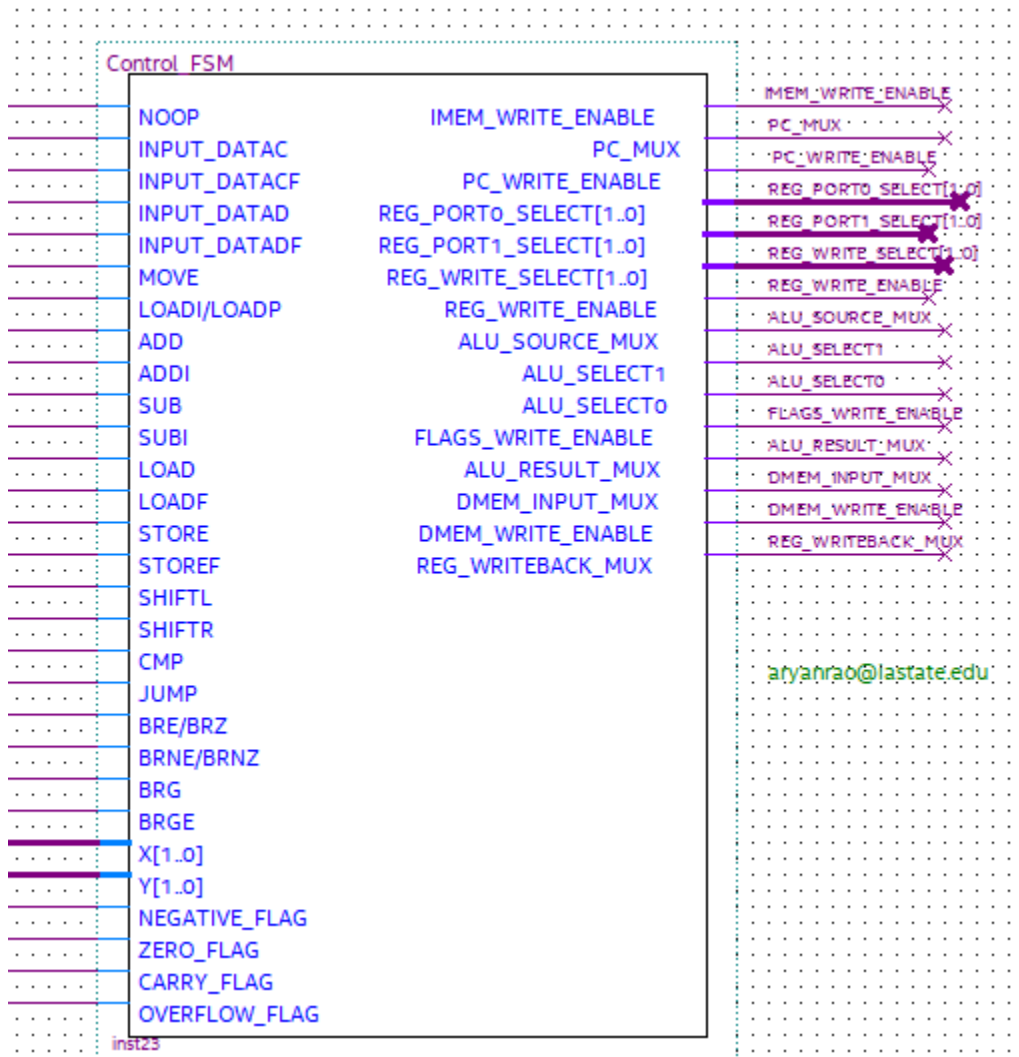
Q8. Find the circuit that outputs the signal **DMEM_WRITE_ENABLE** and then answer the following:

- In which block is this circuit located?
Located inside Control_FSM
- What is the Boolean expression for this signal?
(STOREF) or (STORE) or (INPUT_DATAF) or (INPUT_DATAD)



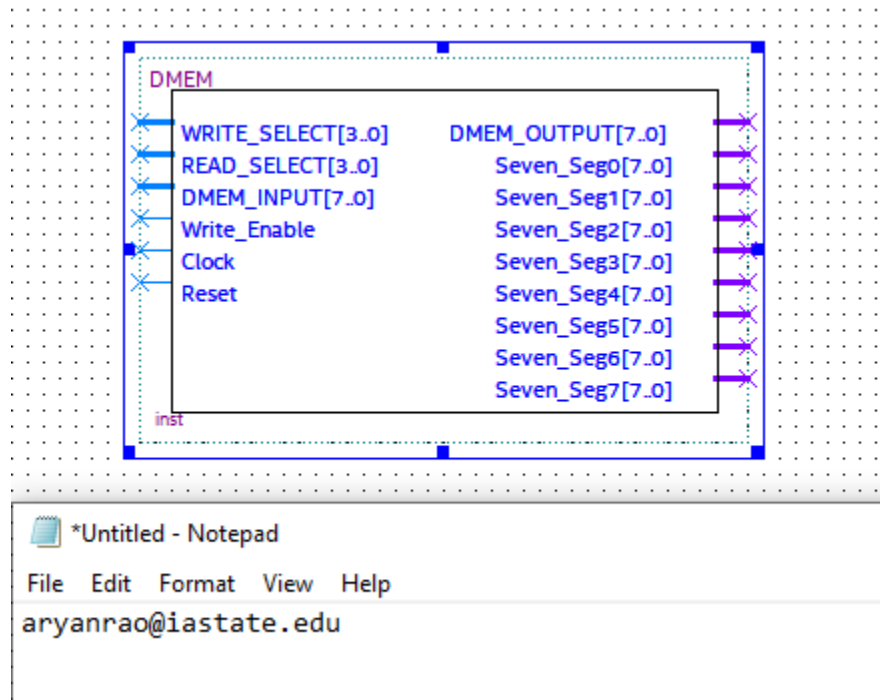Q9. Examine the **DMEM** box and answer the following:

- What are the names of the control lines for this box?
There is 1 Reset, 1 Clock, 1 DMEM_WriteEnable for a total of 3 control lines.(C17)
- What the high-level component is used to store the data?
A register file with 16- registers each 8-bits wide
- What is the size of the data memory in bytes?
16 bytes



Q10. Find the **flags register** and answer the following:

- How many flags does it store?

Stores 4 flags


- What are the names of these flags?

ZeroFlag

NegativeFlag

OverFlowFlag

CarryFlag

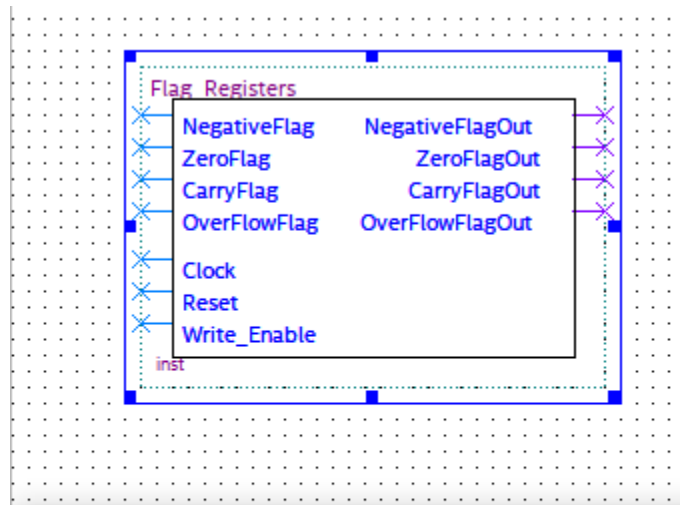

*Untitled - Notepad

File Edit Format View Help

aryanrao@iastate.edu

EC Lab Answer Sheet

Part 2: PONG. Take a cellphone picture of the board as you are playing the game. Selfies are OK too as long as the game is visible in the background 😊

