

HOMEWORK 9


P1. a) A. Sign = 0, Exponent = 10000011, Mantissa = 011000...0
 +ve 29

B. Sign = 1, Exponent = 10000101, Mantissa = 11111000...0
 -ve 17


C. Sign = 1, Exponent = 10000100, Mantissa = 10101000...0
 -ve 18

D. Sign = 0, Exponent = 0111111, Mantissa = 10011001100110011001101
 +ve


B.)

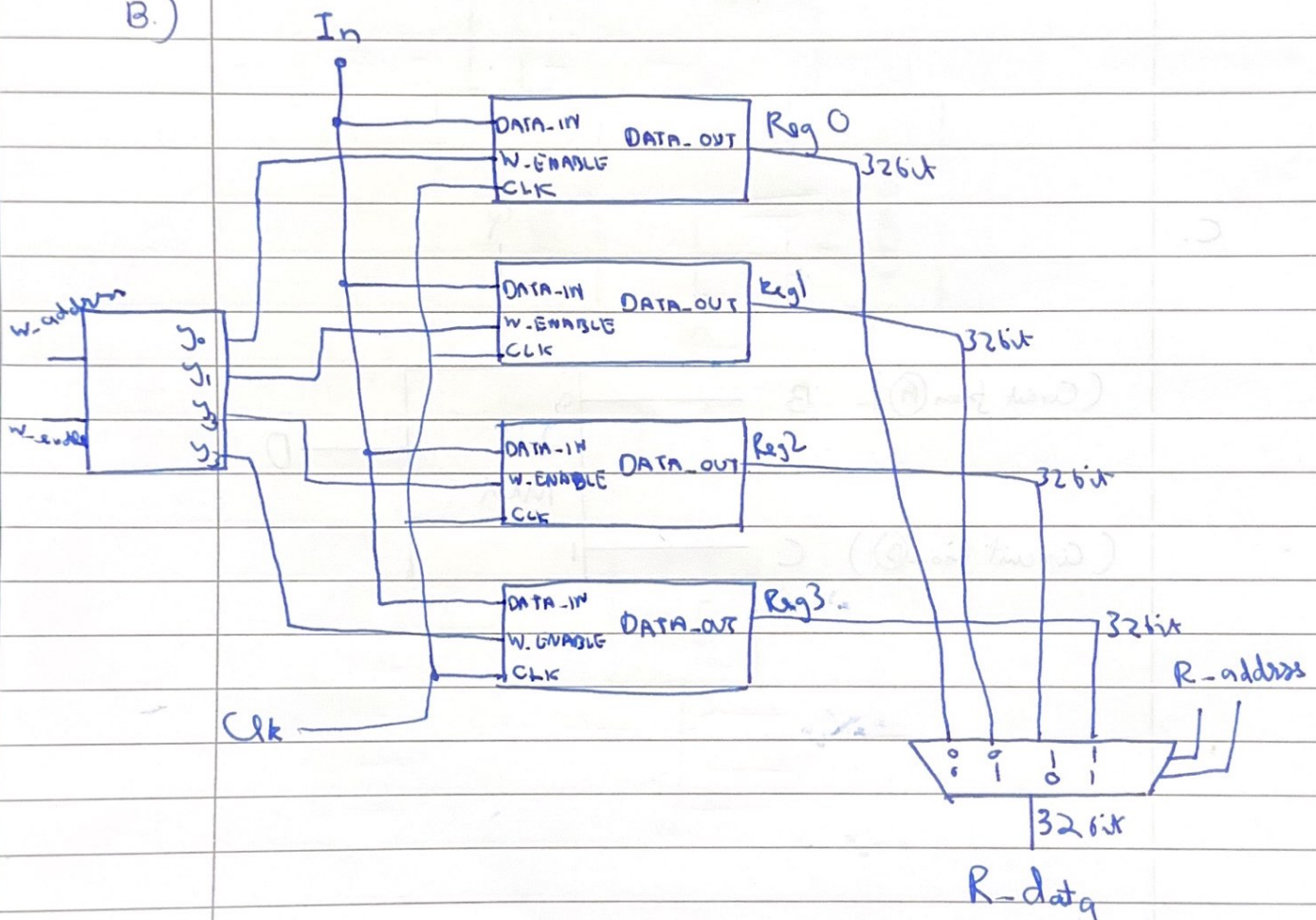

C. a.)

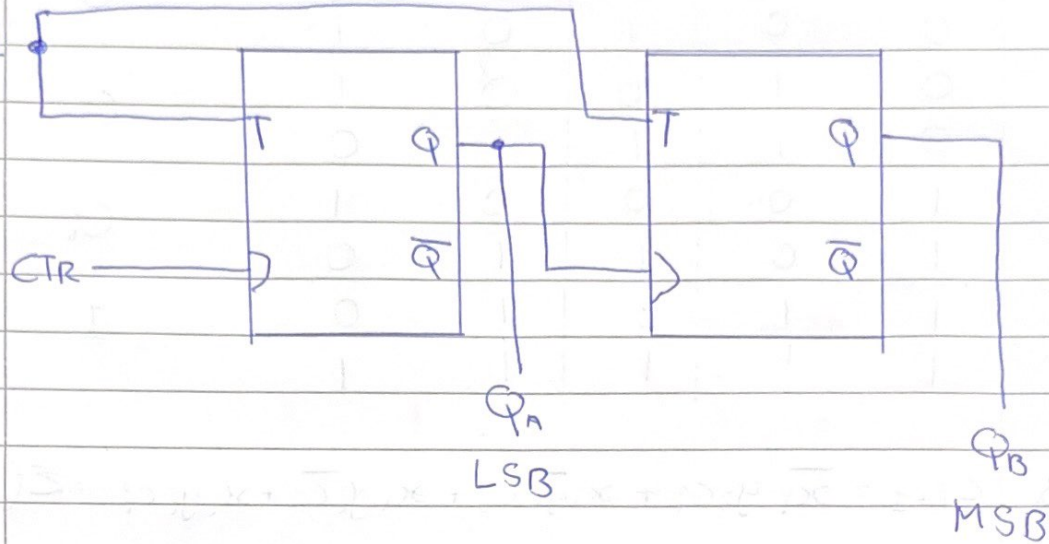

b.)

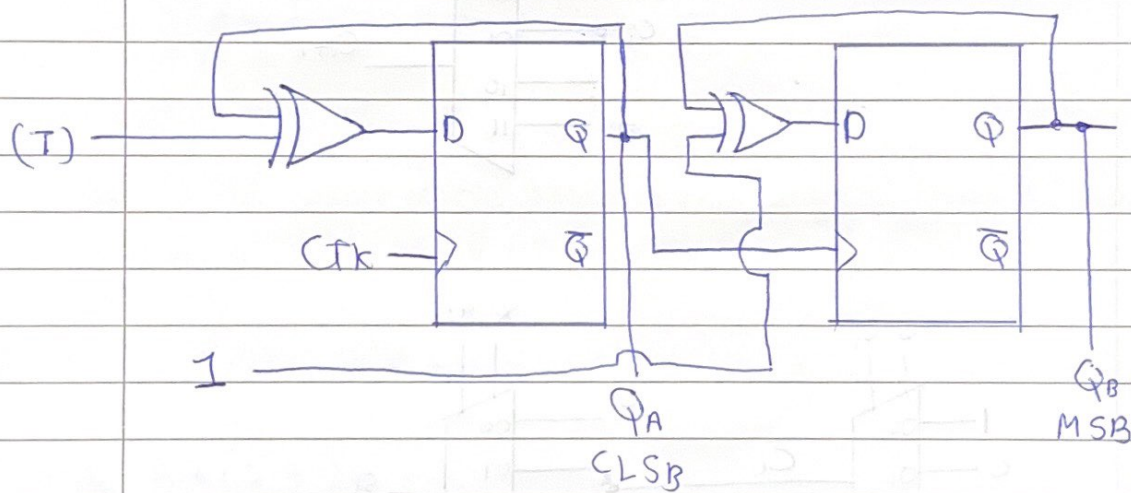



//_

P2. A	x_i	y_i	c_i	C_{i+1}	S_i	C_{i+1}	S_i
	0	0	0	0	0	0	C_i
	0	0	1	0	1		
	0	1	0	0	1	C_i	$\overline{C_i}$
	0	1	1	1	0		
	1	0	0	0	1	C_i	$\overline{C_i}$
	1	0	1	1	0		
	1	1	0	1	0	1	C_i
	1	1	1	1	1		


B. $C_{i+1} = \overline{x_i} y_i c_i + x_i \overline{y_i} c_i + x_i y_i \overline{c_i} + x_i y_i c_i = \Sigma(3, 5, 6, 7)$

$S_i = \overline{x_i} \overline{y_i} c_i + \overline{x_i} y_i \overline{c_i} + x_i \overline{y_i} \overline{c_i} + x_i y_i c_i = \Sigma(1, 2, 4, 7)$


C.

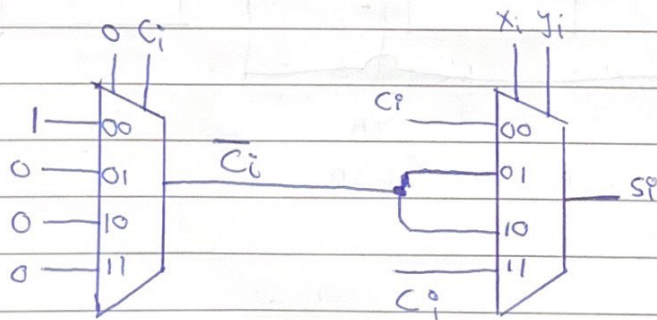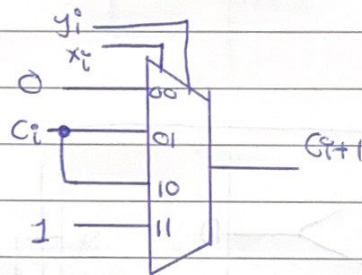


P3. A.

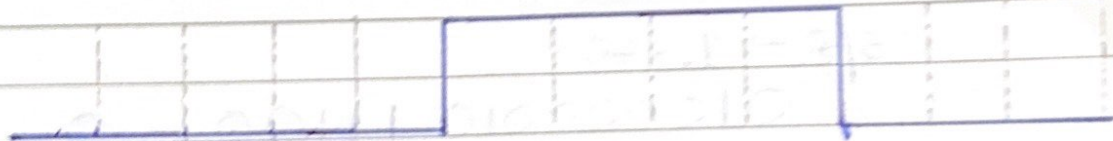


B.

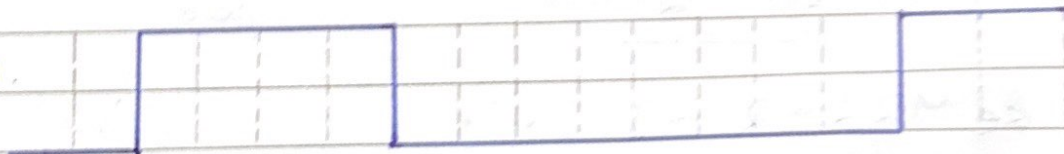

C.

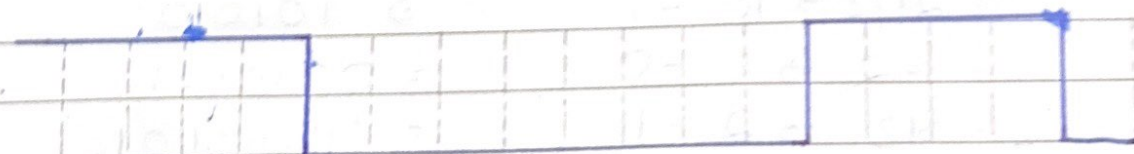

D.

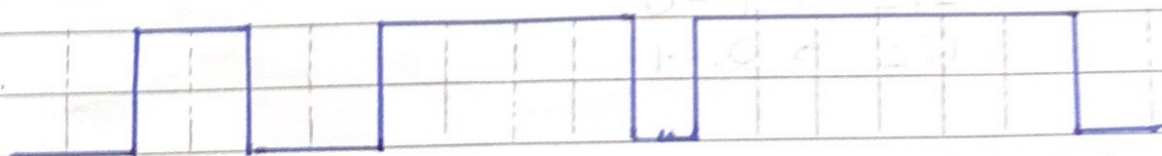

P4. a) $163/2 \rightarrow 81-1$

$81/2 \rightarrow 40-1$

$40/2 \rightarrow 20-0$

$20/2 \rightarrow 10-0$

$10/2 \rightarrow 5-0$

$5/2 \rightarrow 2-1$

$2/2 \rightarrow 1-0$

$1/2 \rightarrow 0-1$

$\Rightarrow 10100011$

$= (110100011)_2 = -163_{10}$

b) $11000001100010000000000000000000$
 $-ve \ 2^{131-128} (1+0.0625)$

$= (-1) \times 2^4 \times (1.0625) = -17_{10}$

c. $15/8 \rightarrow 1.875$

= $0 \mid 10000010 \mid 1100 \dots 0$

tr

$2^{130-127}$

20 ds

— / — / —
150

d. $53/2 \rightarrow 26 \rightarrow 1$

$26/2 \rightarrow 13 \rightarrow 0$

$13/2 \rightarrow 6 \rightarrow 1$

$6/2 \rightarrow 3 \rightarrow 0$

$3/2 \rightarrow 1 \rightarrow 1$

$1/2 \rightarrow 0 \rightarrow 1$

$= 110101$

$= 00110101$

$\Rightarrow (11001011_2)$

$$42/2 \rightarrow 21 - 0$$

$$21/2 \rightarrow 10 - 1$$

$$10/2 \rightarrow 5 - 0$$

$$5/2 \rightarrow 2 - 1$$

$$2/2 \rightarrow 1 - 0$$

$$1/2 \rightarrow 0 - 1$$

$$\Rightarrow 101010$$

$$= 00101010$$

$$= (11010101_2)$$

P5. 2' Complement Range:

$$-2^{N-1} \text{ to } +2^{N-1}-1$$

$$2^{N-1}-1 = 25$$

$$-2^{N-1} = -24$$

$$\text{at } N=5, 2^4 = 24$$

$$16 < 24 \text{ (NOT SATISFIED)}$$

$$\text{at } N=6 = 2^5 = 24, 32 > 24 \text{ (SATISFIED)}$$

\therefore Size of Register = 6 bits.

A. Size of LD-DATA bus = 6 bits

B. Width of each register = 6 bits


C. Width of RA bus \rightarrow 32 registers \rightarrow 5 bits

D. Width of WA bus \rightarrow 6 bit registers \rightarrow 5 bits

E. $32 \times 5 = 160$ DFF's


F. 5-32 Decoder is used

P6. a)

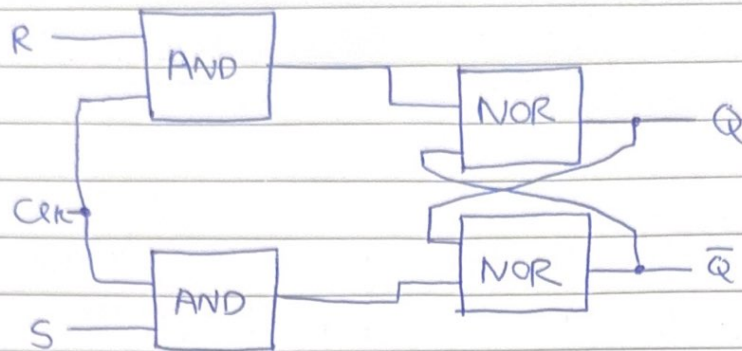

Name : Gated Latch with NOR Gates

b)

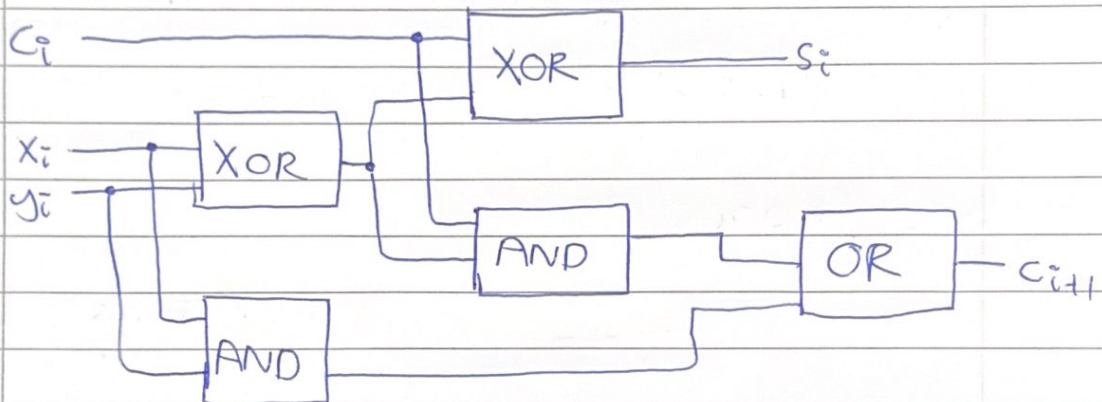

Name : FULL ADDER